

Assignment

EEE101


Section 2

Date of Submission: 5.5.26, 11.00 PM


Total Marks: 45

X: Second last digit of ***ID***


Question 1: Using Superposition Theorem, determine the current I_1 and V_1 . [CO2-PO-a, P1, P3][20]

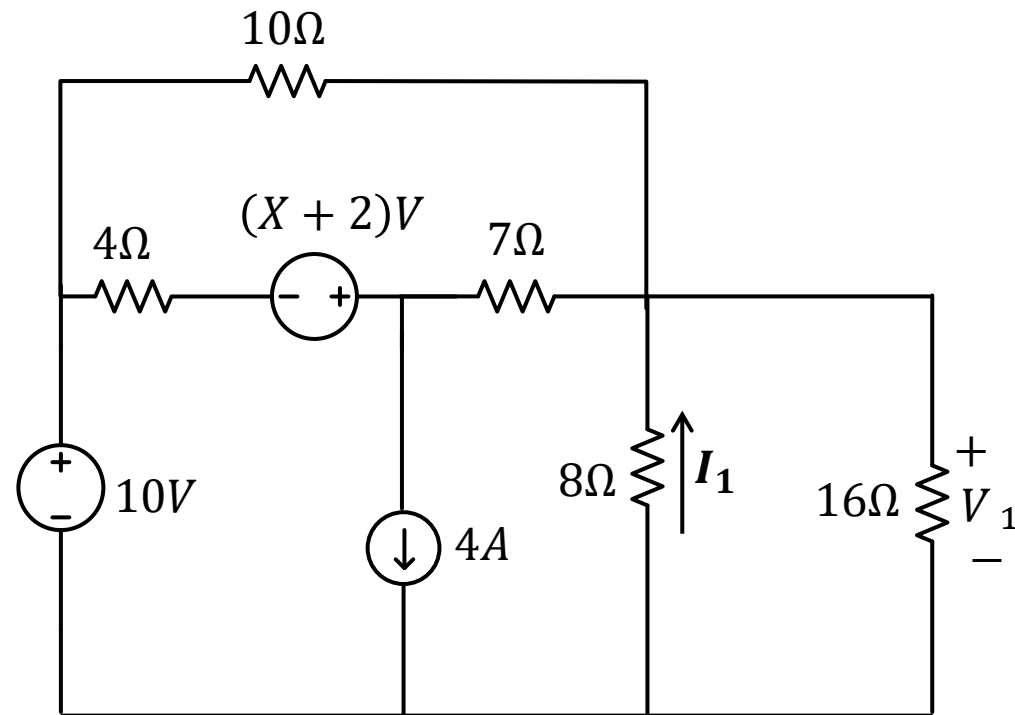

Question 2: Use repeated source transformations, reduce the circuit to a form which is single series circuit and then determine current I_o . [15]

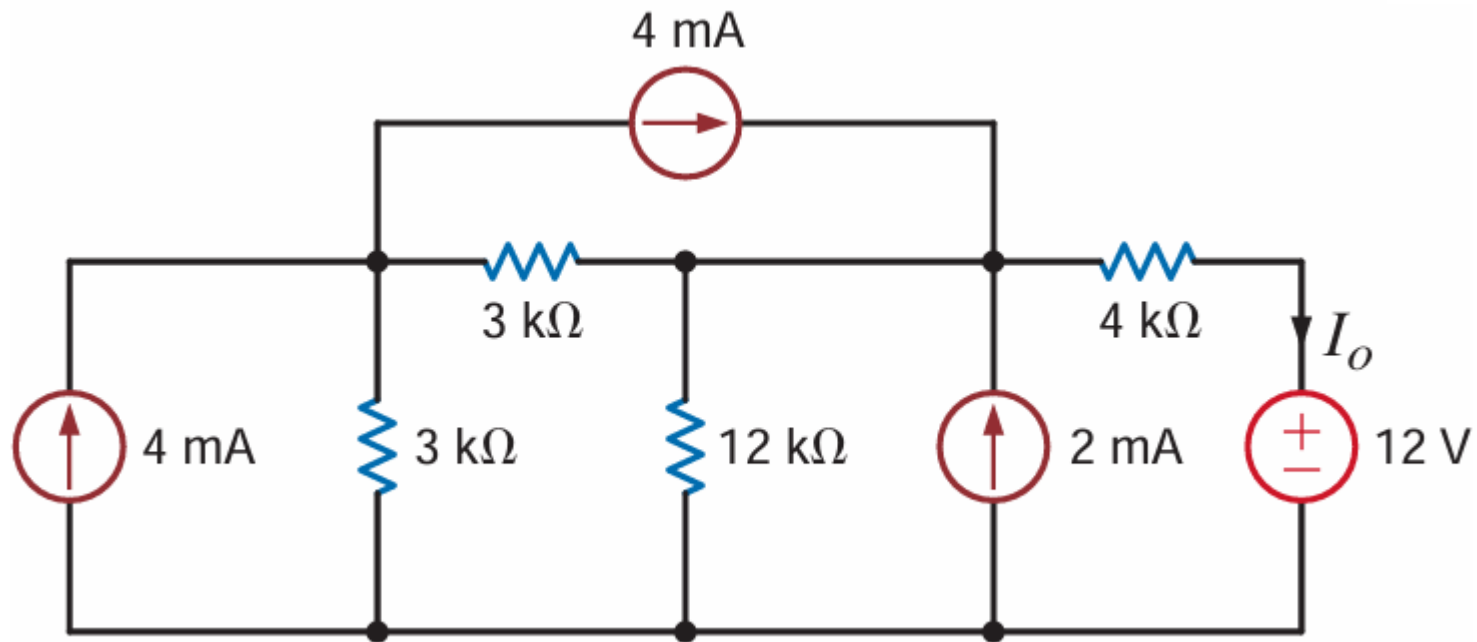

Question 3: Calculate the value of R_L such that it absorbs the maximum power and find the maximum power transferred to R_L . [CO2-PO-a, P1, P3][15]

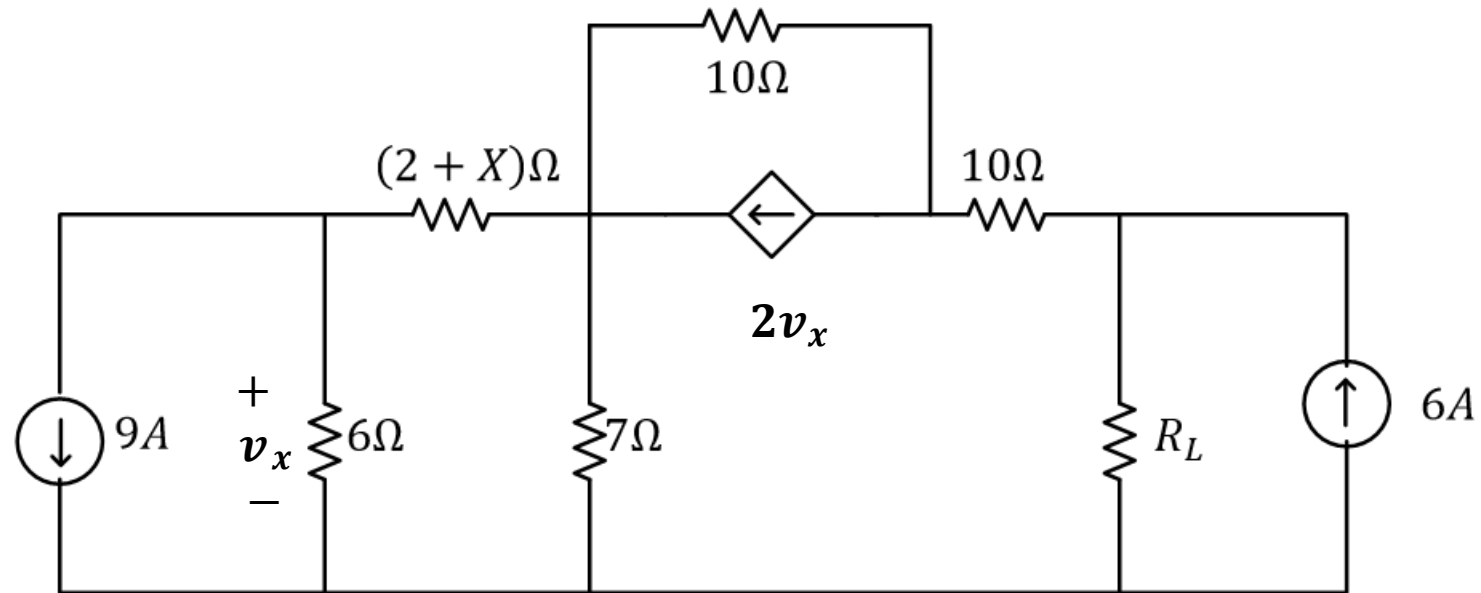

Question 4: The switch has been closed for a long time and is open at $t=0$, Determine the expression for $v_{ab}(t)$ for $-\infty < t < \infty$. [CO3-PO-a, P1, P3][20]

