
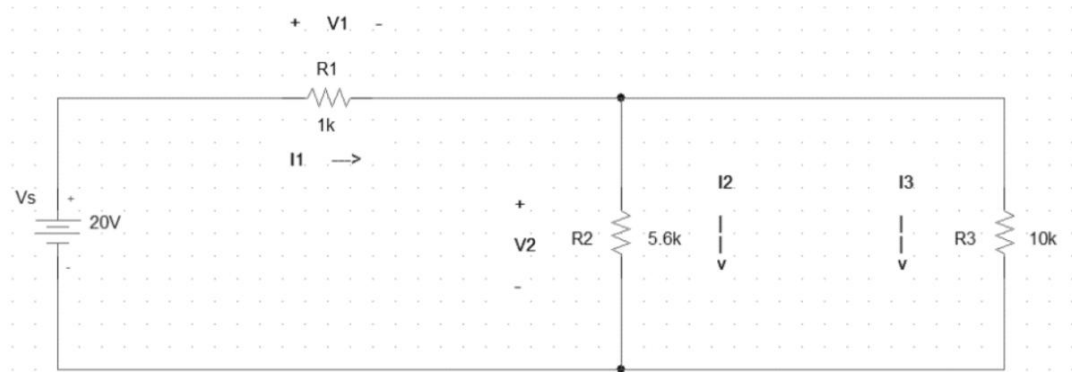


Report Task (Experiment 4)

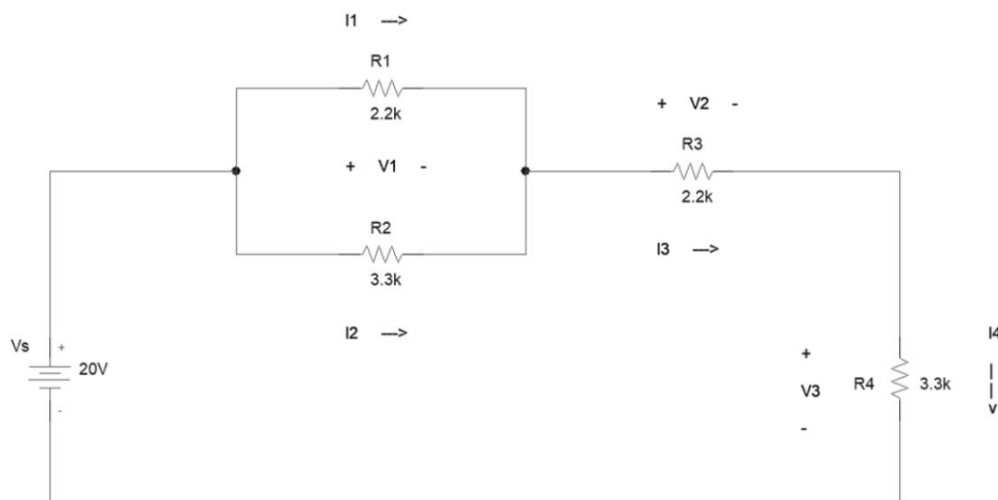1. Verify KCL and KVL for the following circuit:



2. Determine the voltage across and the current through all resistors in the following circuit:



3. Verify the Superposition Theorem for voltage V_4 in the following circuit:

