
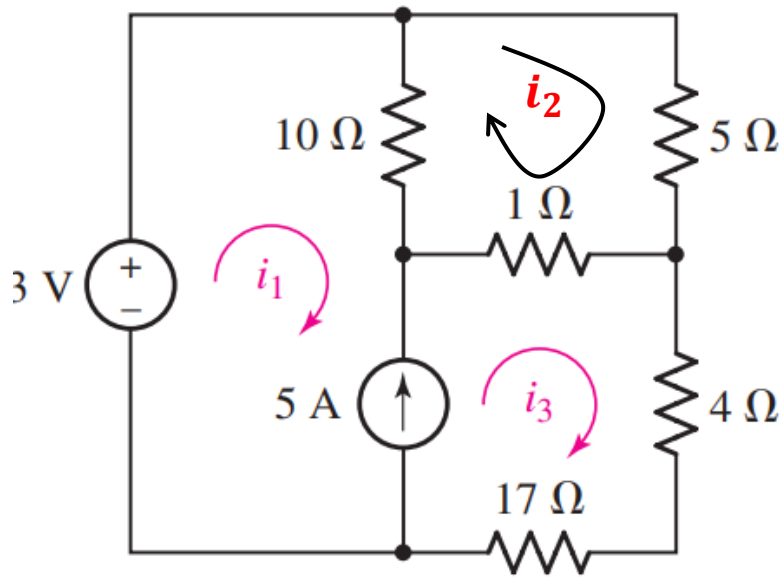


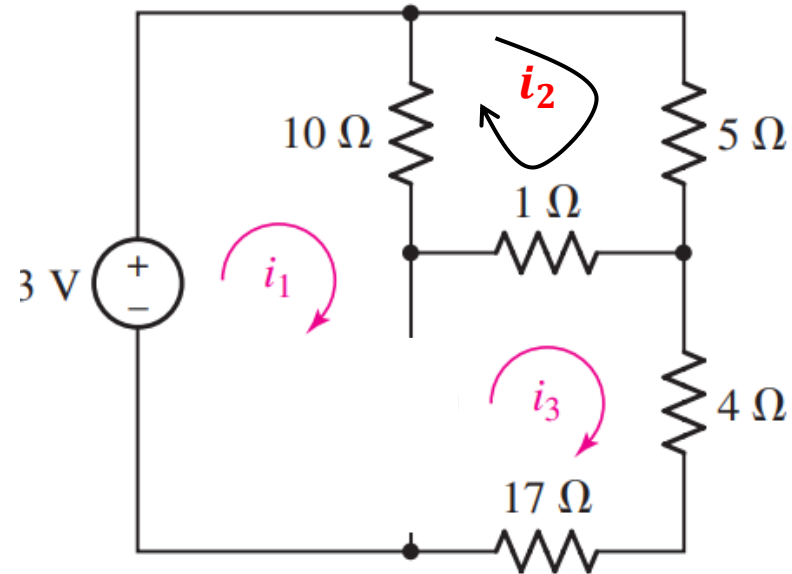Write the supermesh equation in the circuit given below:




Steps

1. Assign mesh currents: i_1 , i_2 and i_3
2. Redraw the circuit opening the current sources to obtain super mesh.
3. Apply KVL around the supermesh.



Steps

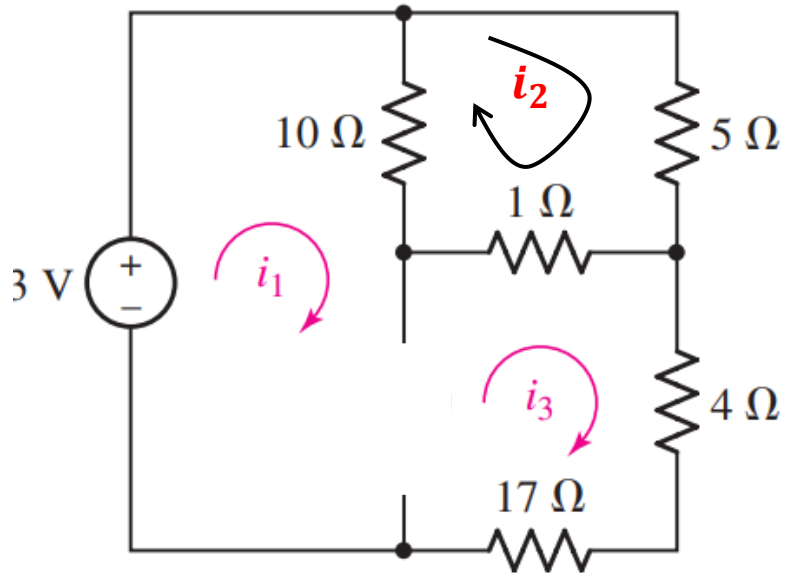1. Assign mesh currents: **i_1 , i_2 and i_3** .
2. Redraw the circuit opening the current sources to obtain super mesh.
3. Apply KVL around the supermesh.



KVL around the supermesh

$$3 - 10(i_1 - i_2) - 1(i_3 - i_2) - 4i_3 - 17i_3 = 0$$