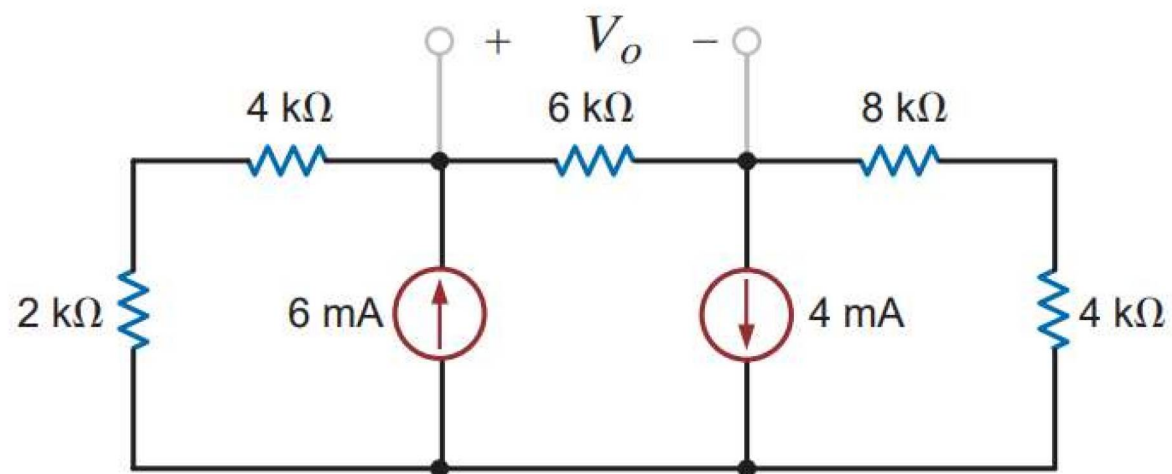


5.9 Find V_o in the network in Fig. P5.9 using superposition.



Find V_o in the circuit in Fig. P5.12 using superposition.



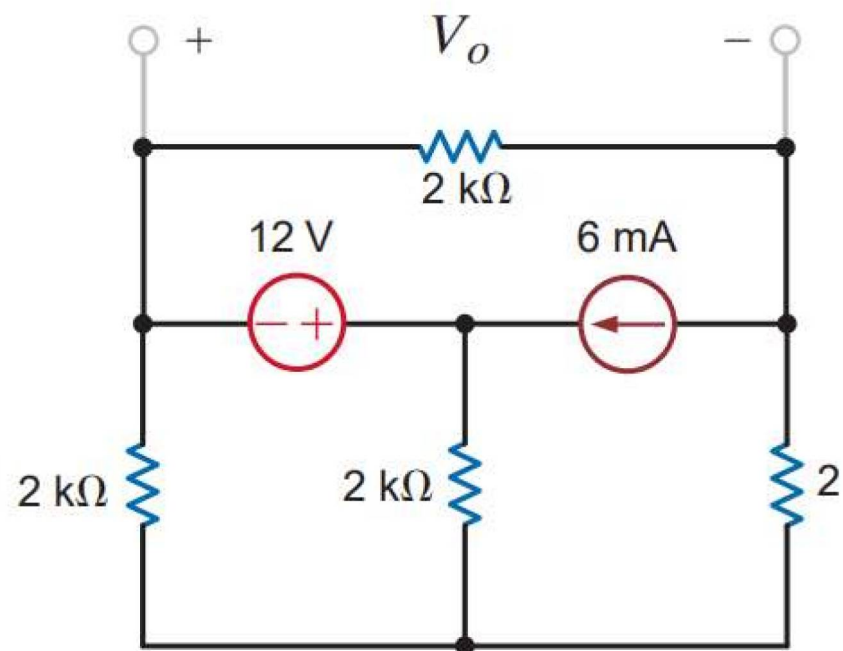
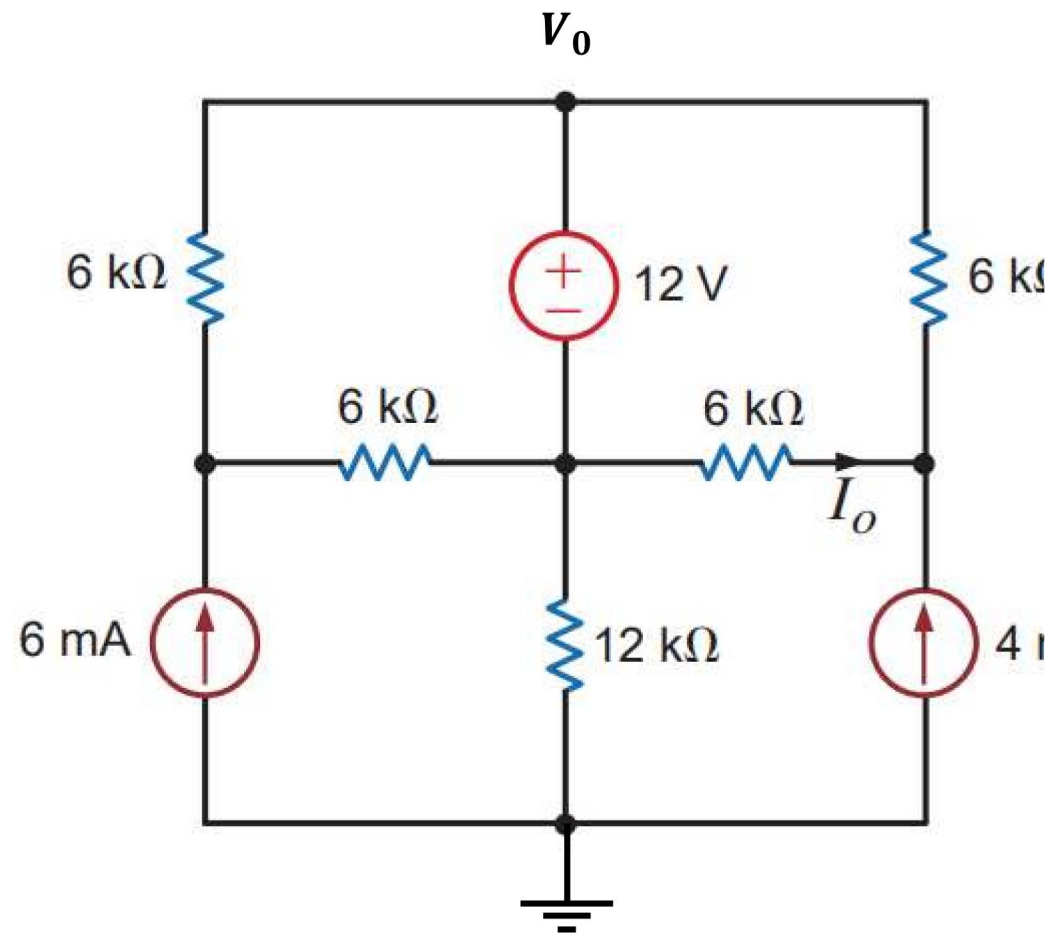
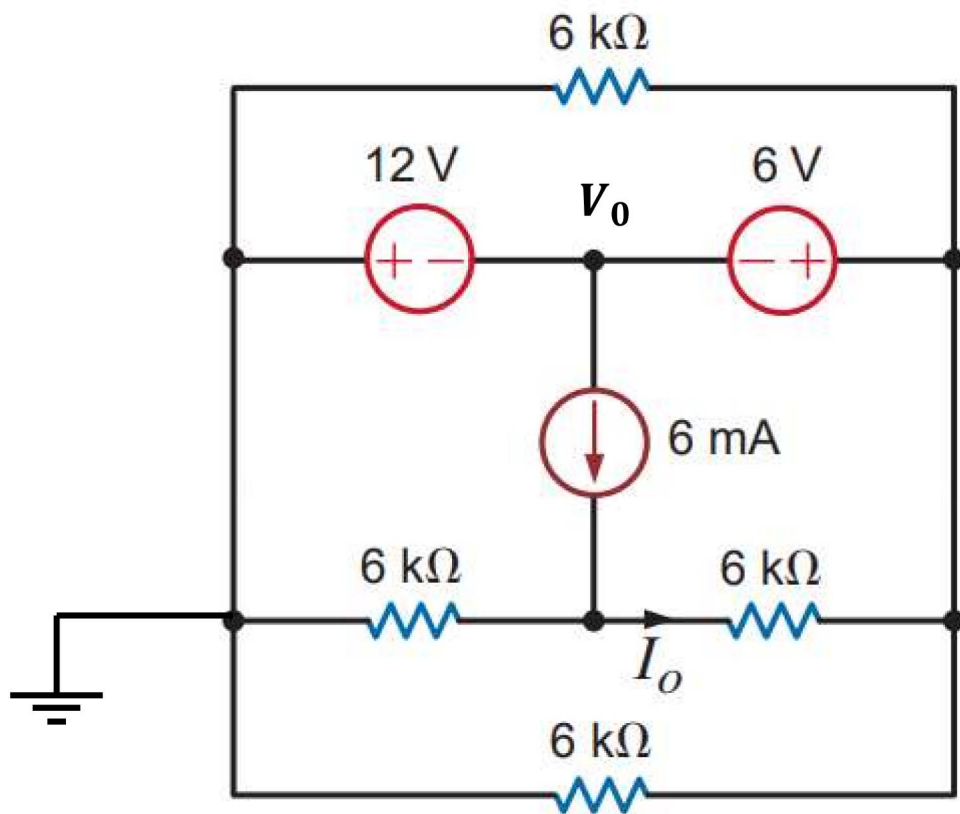


Figure P5.12

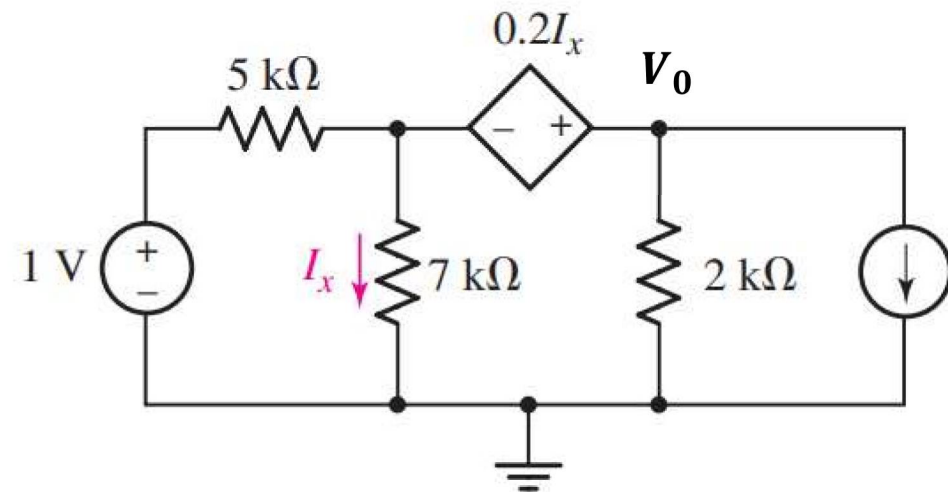


Employ Superposition to determine the labeled current and voltage in the above circuit

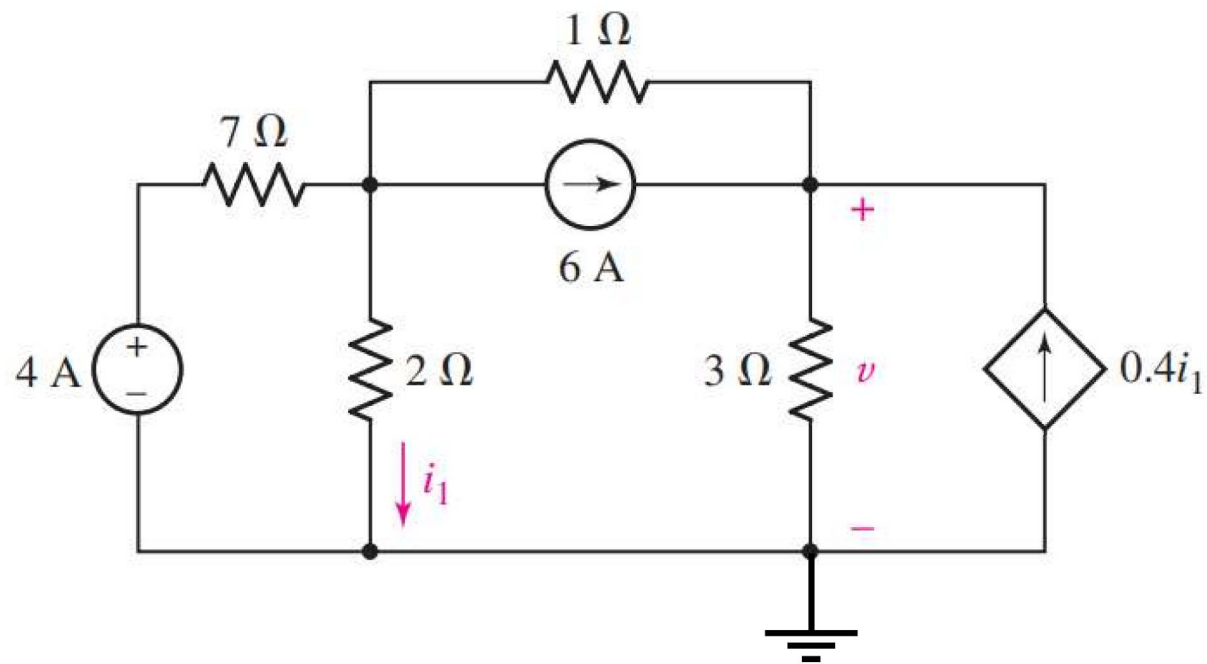Employ Superposition to determine the labeled current and voltage in the following circuit




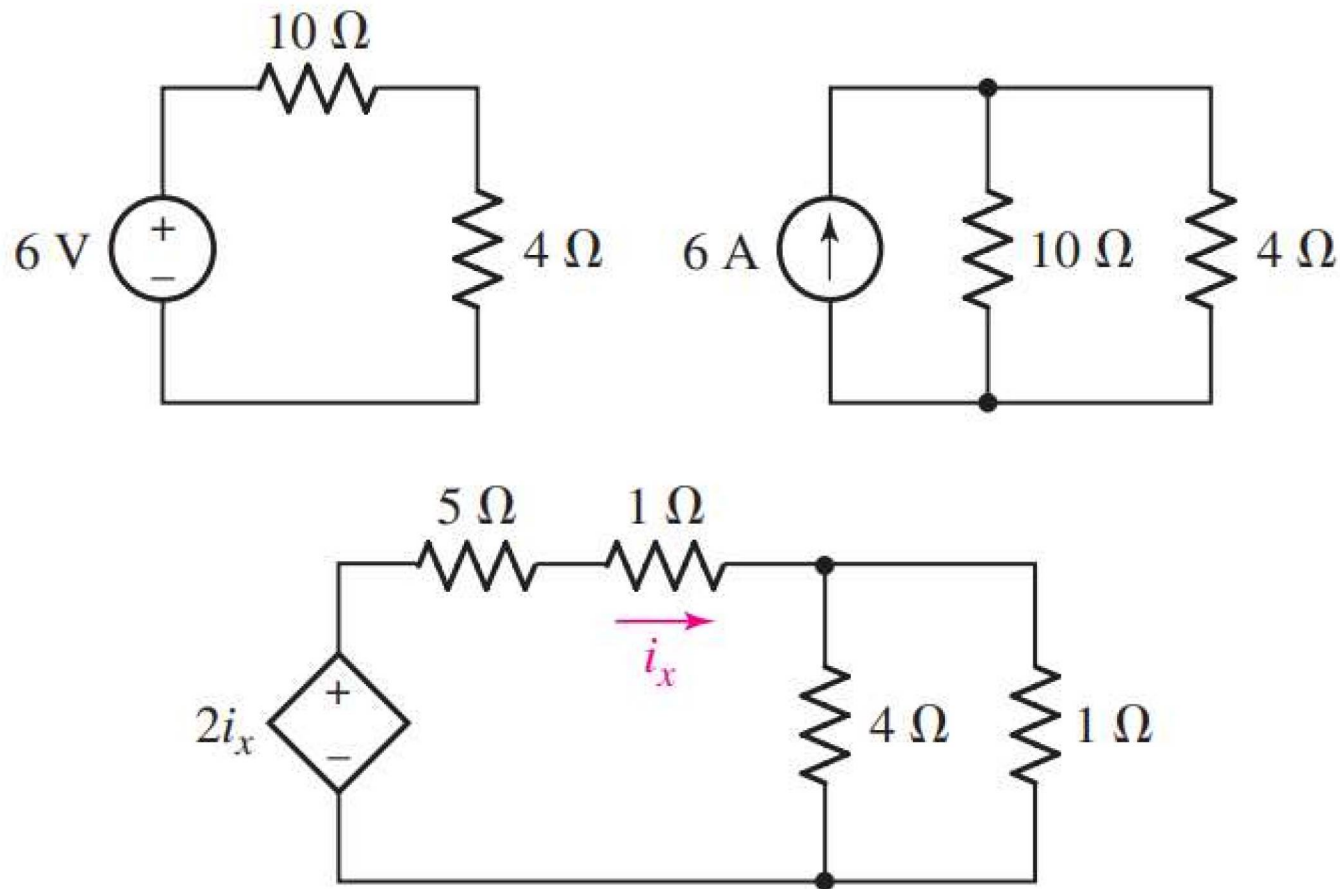13. Perform an appropriate source transformation on each of the circuits depicted in Fig. 5.58, taking care to retain the $4\ \Omega$ resistor in each final circuit.




■ FIGURE 5.58

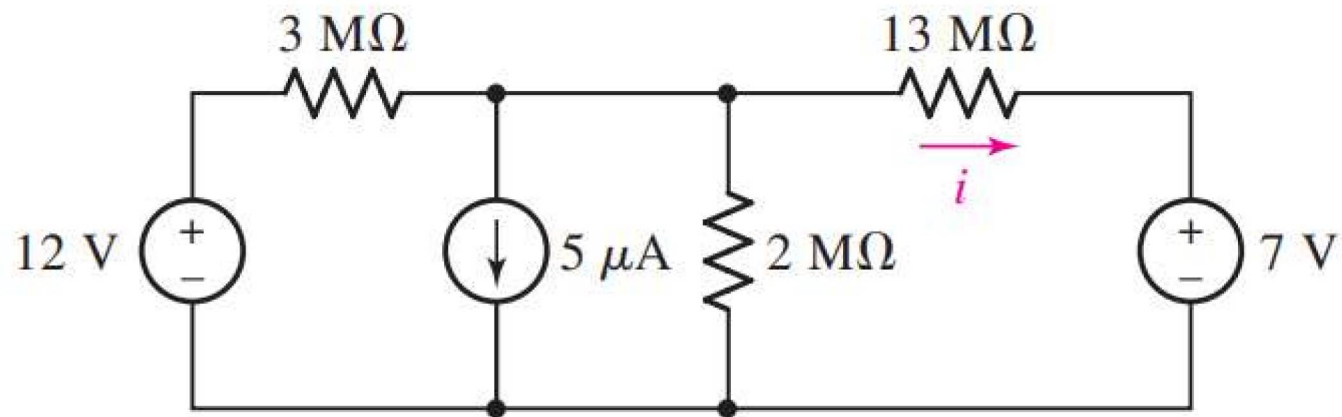
17. (a) Determine the current labeled i in the circuit of Fig. 5.61 after first transforming the circuit such that it contains only resistors and voltage sources.



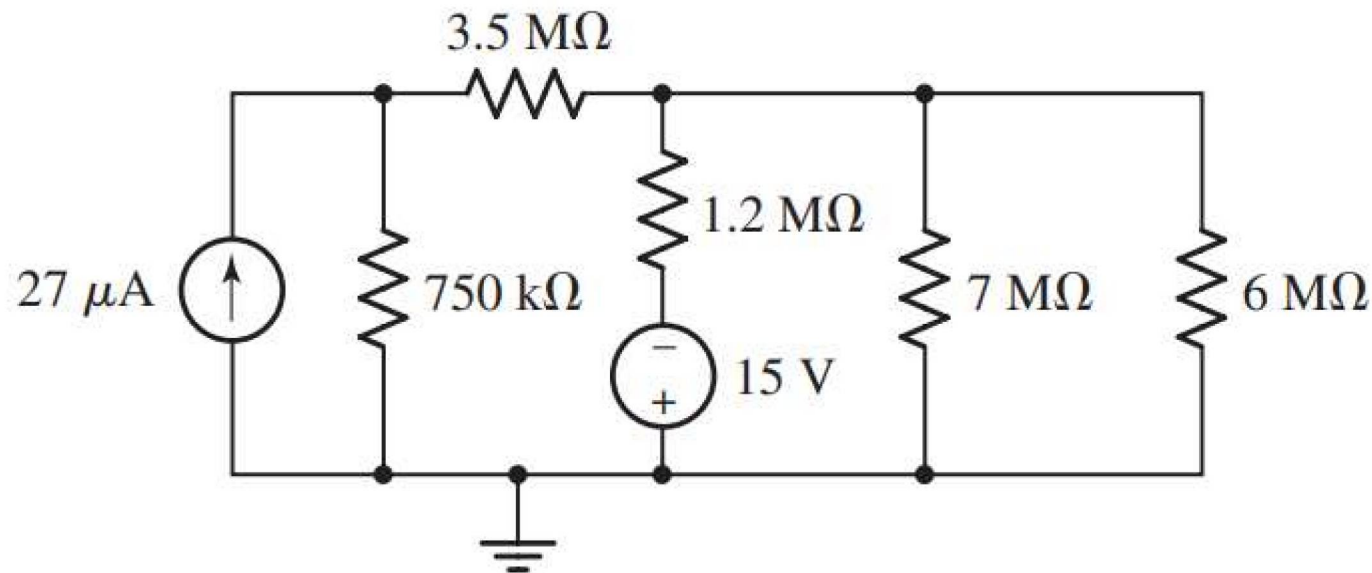18. (a) Using repeated source transformations, reduce the circuit of Fig. 5.62 to a voltage source in series with a resistor, both of which are in series with the $6\text{ M}\Omega$ resistor. (b) Calculate the power dissipated by the $6\text{ M}\Omega$ resistor using your simplified circuit.



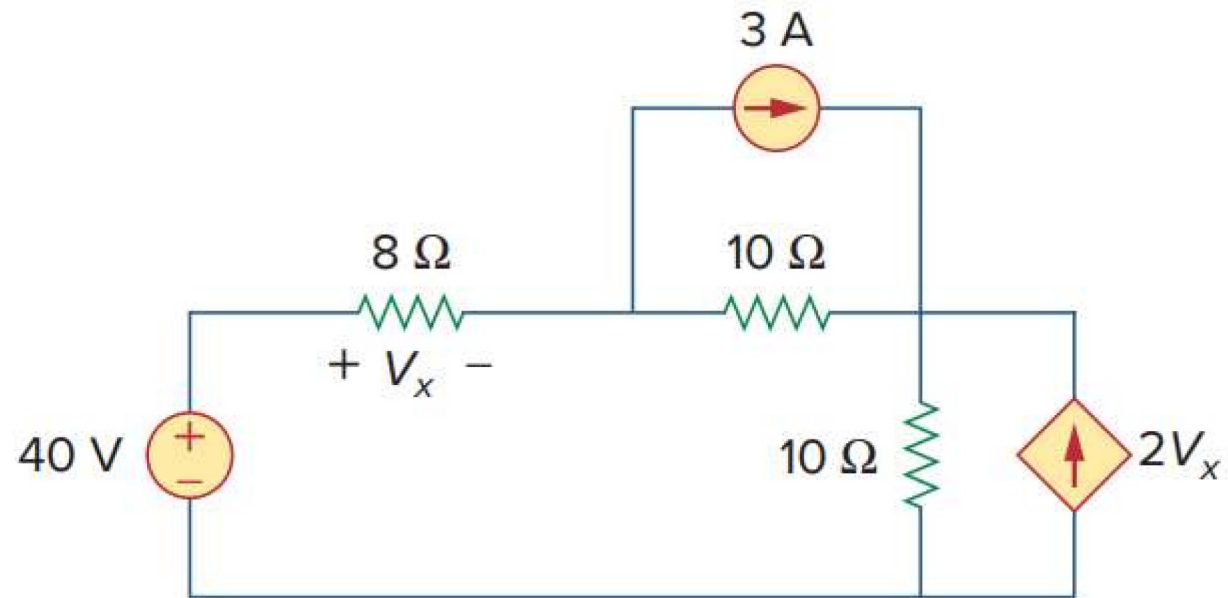4.24 Use source transformation to find the voltage V_x in the circuit of Fig. 4.92.



4.27 Apply source transformation to find v_x in the circuit of Fig. 4.95.

