
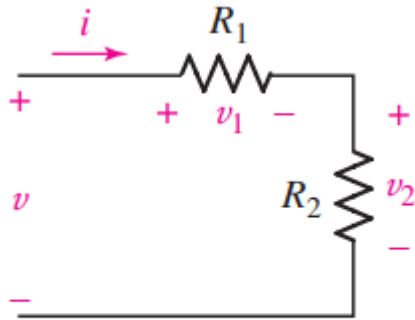



VOLTAGE AND CURRENT DIVISION

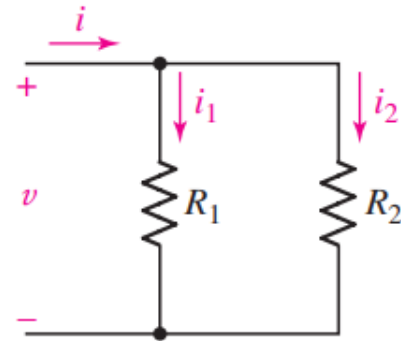


■ **FIGURE 3.34** An illustration of voltage division.



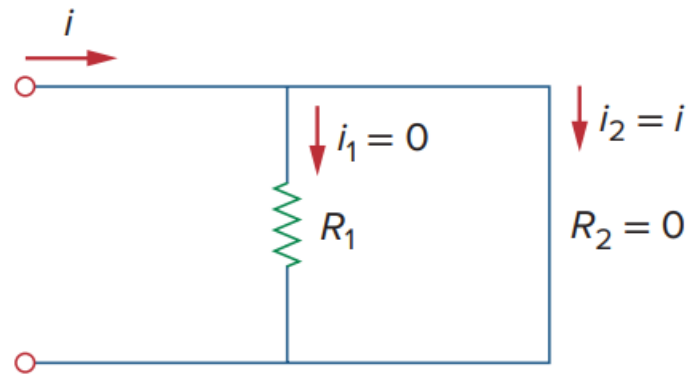
■ **FIGURE 3.37** An illustration of current division.






(a)

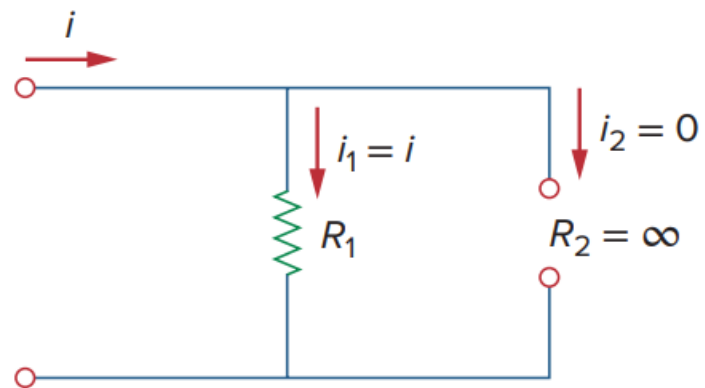


(b)

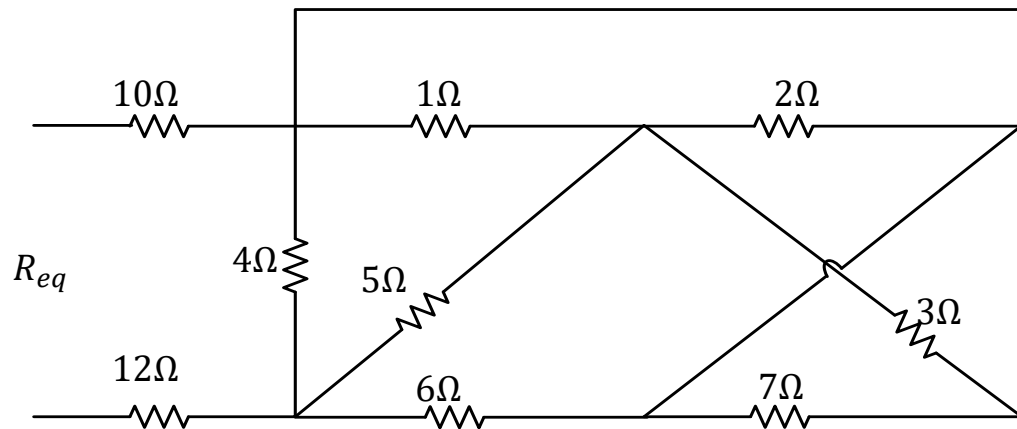

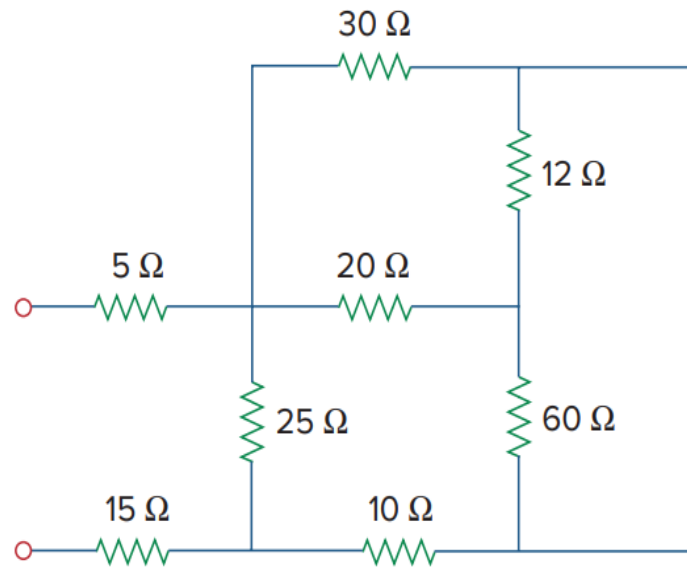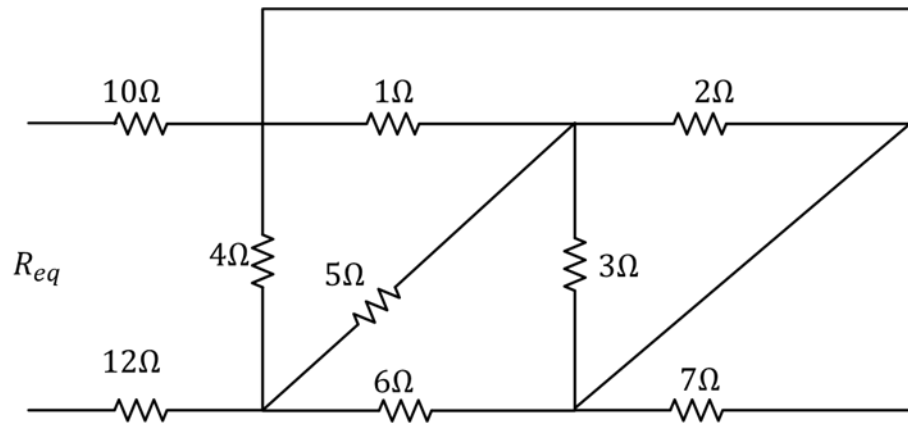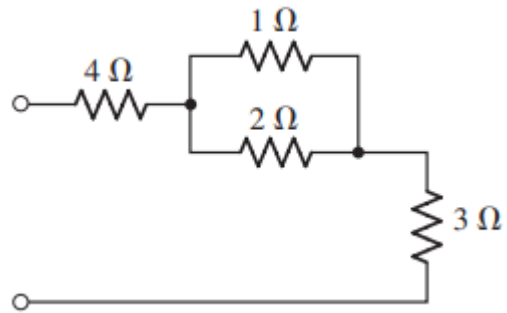


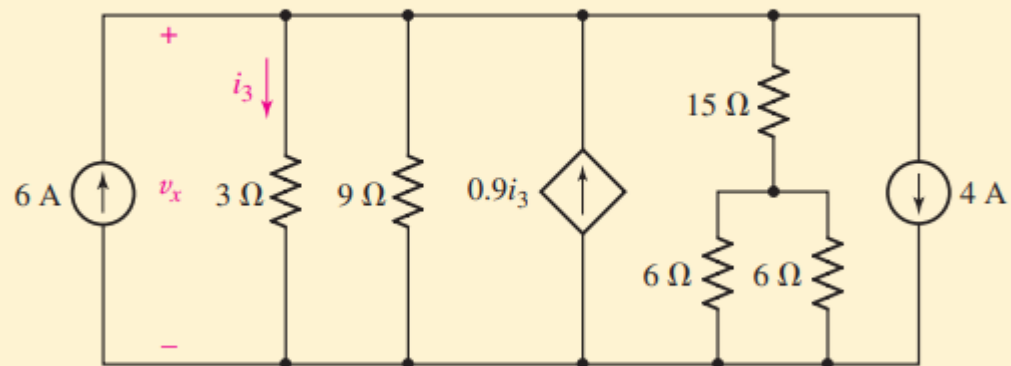Calculate the power and voltage of the dependent source in Fig. 3.31a.



(a)

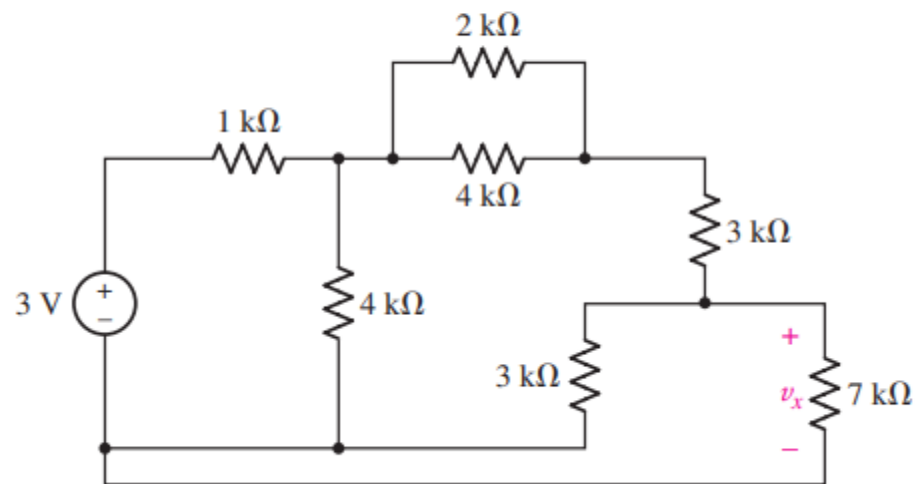57. In the circuit of Fig. 3.93, only the voltage v_x is of interest. Simplify the circuit using appropriate resistor combinations and iteratively employ voltage division to determine v_x .



■ FIGURE 3.93