
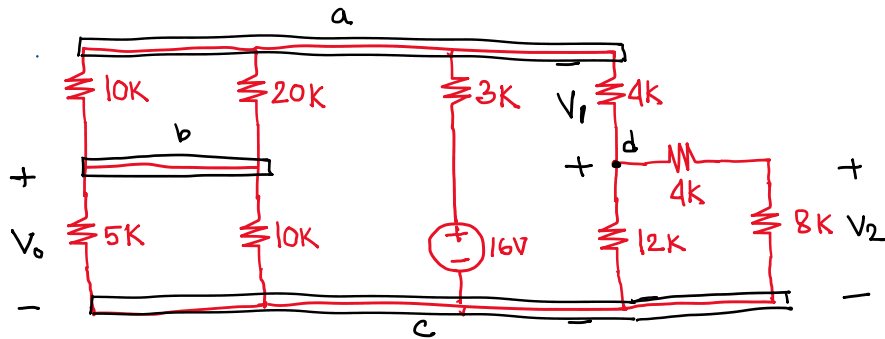


Equivalent_Ckt_3


Tuesday, November 4, 2025 5:56 PM

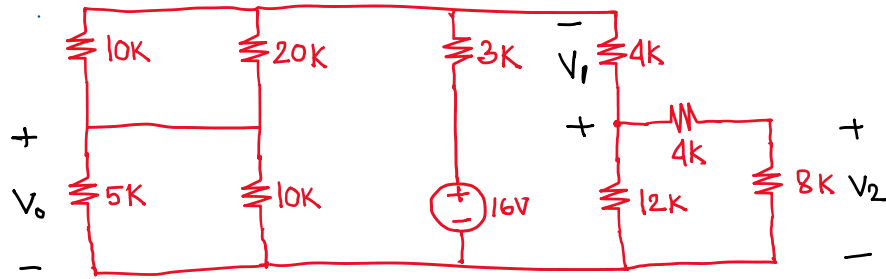


Between node a & b: $10K \parallel 20K$
 $= \frac{10 \times 20}{30}$
 $= 6.67K$

Between node c & b: $5K \parallel 10K$
 $= 3.33K$

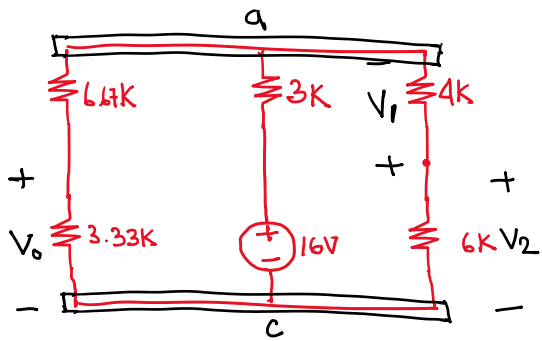Between node d & c: $12K \parallel (4K + 8K)$ ← Series
 $= 12K \parallel 12K$
 $= 6K$



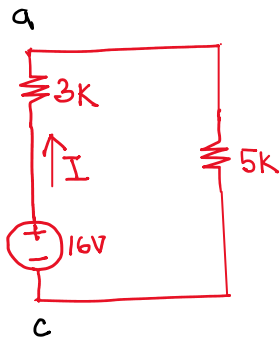Between node a & c: $(6.67K + 3.33K) \parallel (4K + 6K)$
 $= 10K \parallel 10K$
 $= 5K$



$I = \frac{16}{8} = 2mA$